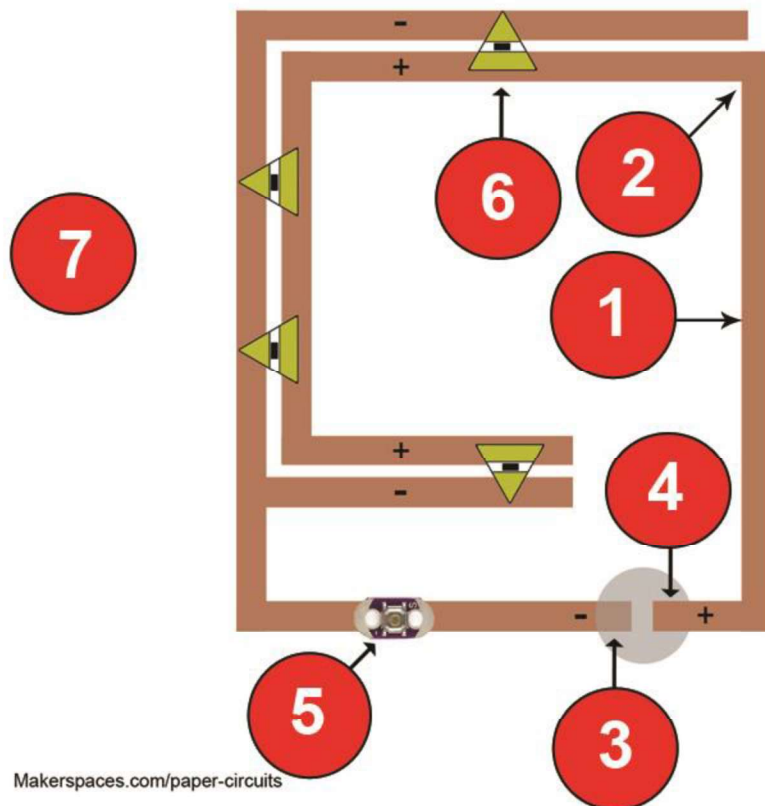


Firefly Jar



- 3v +

Firefly Circuit



Materials:

Copper Tape - 1/4"
Battery - CR2032 - 3v
Transparent Tape
LilyPad Button Switch
Circuit Stickers - yellow

Tools:

Scissors
Scoring Tool
X-Acto Knife

Time Required:

30 minutes

Steps:

- 1 Apply copper tape to trace line. Smooth with finger. Allow a gap for switch and circuit stickers.
- 2 Fold copper tape at all corners. Try to maintain a continuous strip with no cuts.
- 3 Place battery on top of copper tape with negative (-) facing down.
- 4 Stick end of copper tape to the top of battery (+)
- 5 Mount LilyPad switch using clear tape. Make sure there is a gap in the copper tape below switch.
- 6 Stick Circuit Stickers to copper tape. Wide side goes on (+) of copper tape.
- 7 Place firefly overlay directly over this circuit template.

Firefly Circuit

