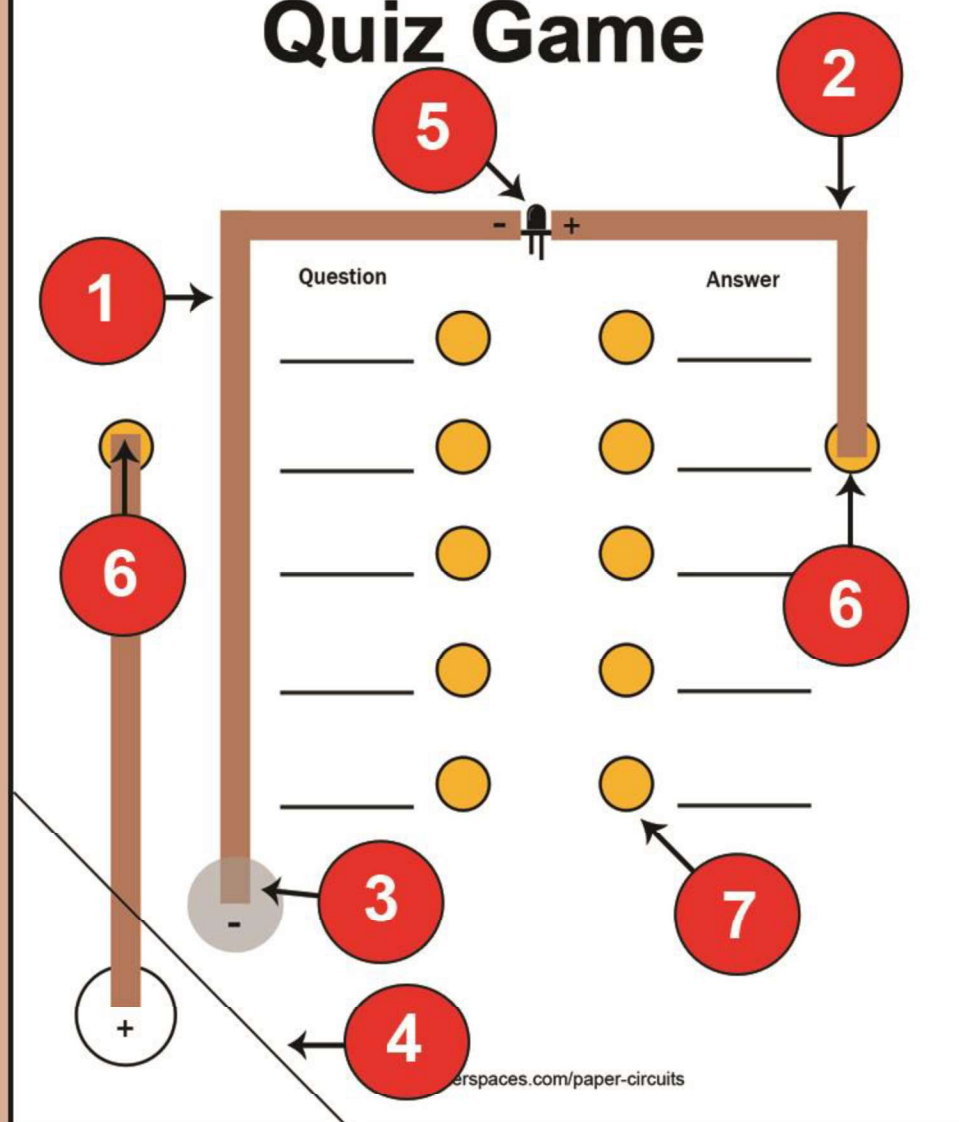




# Quiz Game

- 3v +

# Quiz Game



## Materials:

Copper Tape - 1/4"  
 Battery - CR2032 - 3v  
 Transparent Tape  
 LED - 5mm or 10mm  
 Paperclip / Binder Clip  
 Brass Brad  
 Alligator Clips/Leads  
 Circuit Stickers (optional)

## Tools:

Scissors  
 Scoring Tool  
 X-Acto Knife

## Time Required:

30 minutes

## Steps:

- 1 Apply copper tape to trace line on template. Smooth with finger. Allow a gap for LED.
- 2 Fold copper tape at all corners. Try to maintain a continuous strip with no cuts.
- 3 Place battery on top of copper tape with negative (-) facing down.
- 4 Fold corner of template along the line. Using a scoring tool helps with this process. Use paperclip to secure corner.
- 5 Bend legs of LED at a 90° angle. Use clear tape to secure LED to copper tape. Long leg of LED goes on positive.
- 6 Push brad thru template & copper from the backside. Attach alligator clip to legs of the brad.
- 7 Push brads from front to back. Connect question to correct answer on back w/ copper. Put clear tape over each path so they don't touch.

# Quiz Game

