11/17/2018 multiwingspan

MultiWingSpan

Home Programming Web Design Computer Science Twisting Puzzles Arduino BBC micro:bit


BBC micro:bit Driving A Motor

Introduction

Circuit

In this circuit you have,

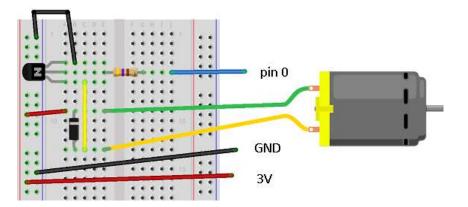- Motor
- 470 Ohm Resistor
- NPN transistor
- Diode 1N4148



Program

We'll turn the motor on when the A button is pressed, otherwise we'll switch it off.

```
from microbit import *
while True:
   if button_a.is_pressed():
        pin0.write_digital(1)
   else:
        pin0.write_digital(0)
   sleep(50)
```

Challenge

Stick to the single motor and go easy when using this much power from the micro:bit. Make a spinning circle out of card and place it on the axle of the motor. Use this in a game, as a pretty colour wheel or as a nice little fan.

BBC Microbit

Collapse All Expand All

- + Block Editor The Basics
- + Block Editor Components
- + Kodu micro:bit Worlds
- + JavaScript Blocks
- + JavaScript Blocks Exercises
- + Blocks Bit:Bot
- + Blocks Bit:Commander
- + MicroPython Starting Off
- + MicroPython Examples
- MicroPython Components
- Microrython Componen
- * Introduction
- ★ Buzzer With MicroPython
- ★ LEDs With MicroPython
- * Connecting micro:bits Together
- * Extra Buttons
- * Knock Sensor
- * Rotary Encoder
- * Potentiometer
- 大 Soft Potentiometer 大 Flex Sensor
- * Tilt Sensor
- * Reed Switch
- * More Buttons
- 大 Temperature Sensor 大 7 Segment Display
- * Reflectance Sensor
- * Driving A Motor
- 🛨 Shift Register
- 🛨 Shifting In
- * Neopixels
- * IR Break Beam Sensor
- * DIY MIDI Out
- * PCF8574A Port Expander
- * 16x2 Character LCD Display
- * SNES Controller
- + MicroPython Breakout Boards
- + MicroPython Exercises
- + MicroPython Pi Accessories
- + MicroPython Bit:Bot
- + MicroPython Bit:Commander
- + MicroPython Projects
- + MicroPython Visual Basic
- + Other Odds & Ends







Pages designed and coded by MHA since 2003 | Valid HTML 4.01(Strict) | CSS